ME 236 / CE 291F / EE 291 Final Project Presentation

A Precompensation Filter for the Telegraph Equation

Tony Dear and Alejandro Schuler

Presentation Outline

Problem statement

- The physical model
- The transfer function

- Preliminary simulations
- Further work

Problem Statement and Motivation

- Consider sending a signal down a transmission line.
- Real lines are not perfect.
 - ▶ Resistance, capacitance, inductance, etc.
- As a result, signals become distorted!




- The telegraph equation is a model for describing the parasitic effects along a line.
- Given the model, can we develop a **filter to pre-compensate** for the signal's degradation?



The Physical Model and Telegraph Equation

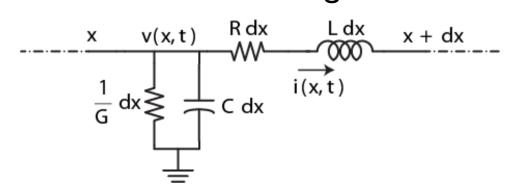- We divide the line into infinitesimal pieces.
- Each piece contains the following elements:



Combining KVL and KCL and eliminating the current yields the telegraph equation:

$$\frac{\partial^2 v(x,t)}{\partial x^2} = LC \frac{\partial^2 v(x,t)}{\partial t^2} + (LG + RC) \frac{\partial v(x,t)}{\partial t} + RGv(x,t)$$

BC's:
$$v(0,t)=u(t)$$
 $v(l,t)=Zi(l,t)=y(t)$



The Laplace Transform

In order to solve the PDE by differential flatness, we apply the Laplace transform:

$$\hat{v}_{xx}(x,s) = LCs^2\hat{v}(x,s) + (LG + RC)s\hat{v}(x,s) + RG\hat{v}(x,s) = \omega(s)\hat{v}(x,s)$$

- where $\omega(s) = LCs^2 + (LG + RC)s + RG$
- ▶ The solution to this 2nd-order ODE is well known:

$$\hat{v}(x,s) = A(s) \cosh\left(\sqrt{\omega(s)}x\right) + B(s) \sinh\left(\sqrt{\omega(s)}x\right)$$

▶ We take the "Laplaced" B.C.s to solve for constants:

$$\hat{v}(0,s) = \hat{u}(s)$$
 $\hat{v}(l,s) = Z\hat{i}(l,s) = -\frac{Z}{R+sL}\hat{v}_x(l,s) = \hat{y}(s)$

Substitution and algebra yield

$$\hat{u}(s) = \left(\cosh(\sqrt{\omega(s)}l) + \frac{R + sL}{Z} \frac{\sinh(\sqrt{\omega(s)}l)}{\sqrt{\omega(s)}}\right) \hat{y}(s)$$



Time Domain Solution

- Assume $G=\mathfrak{g}$ let $\lambda=l\sqrt{LC}$ and $\alpha=R/2L$
- Then we can use the inverse Laplace transforms and various identities to obtain


$$u(t) = \frac{1}{2}e^{-\alpha\lambda} \left(1 - \frac{1}{Z}\sqrt{\frac{L}{C}} \right) y(t - \lambda) + \frac{1}{2}e^{\alpha\lambda} \left(1 + \frac{1}{Z}\sqrt{\frac{L}{C}} \right) y(t + \lambda)$$

$$+ \int_{-\lambda}^{\lambda} \left\{ \frac{R}{4Z\sqrt{LC}} e^{-\alpha\tau} J_0(i\alpha\sqrt{\tau^2 - \lambda^2}) + \frac{e^{-\alpha\tau}i\alpha}{2\sqrt{\tau^2 - \lambda^2}} \left(\lambda - \frac{1}{Z}\sqrt{\frac{L}{C}} \tau \right) J_1(i\alpha\sqrt{\tau^2 - \lambda^2}) \right\} y(t - \tau) d\tau$$



Simulation Paradigm

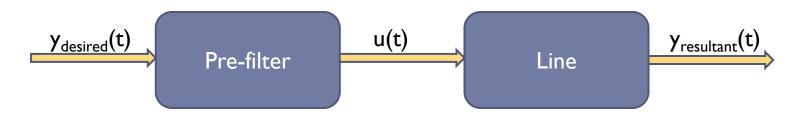We seek to prove the effectiveness of the pre-filter by simulation.




- ▶ Entails two simulations: the pre-filter and the line
 - Prefilter simulation: Computation of the time-domain pre-filter equation (MATLAB)
 - Line simulation: Discretization of the telegraph equation into its "infinitesimal" components and solving the circuit (SPICE)
- Success if $= y_{desired}(t) y_{resultant}(t)$








Pre-filter Simulation Results

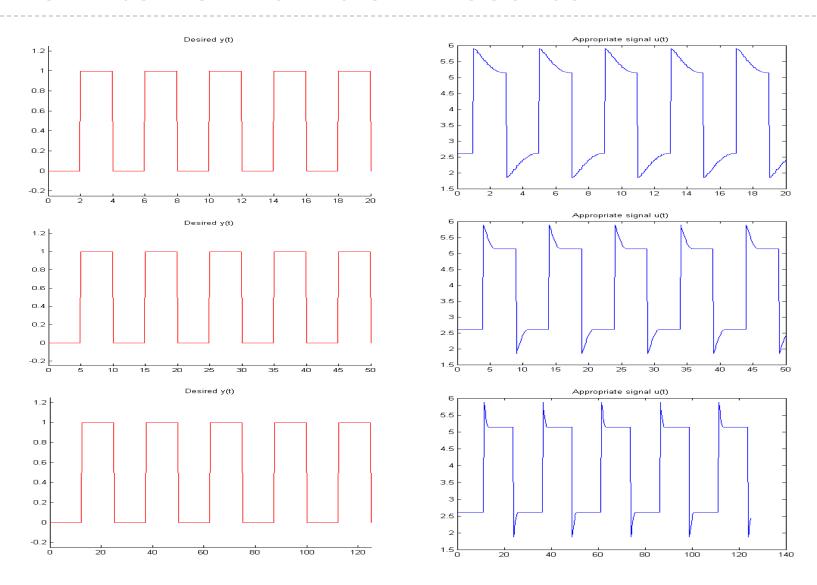



Transmission Line Simulation Work

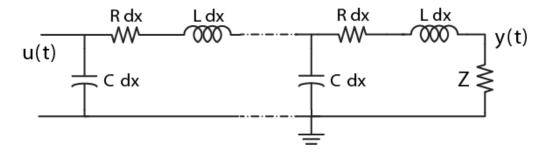- The circuit is set up with N discrete elements (see below).
- ▶ The final element is capped with a load impedance Z.




- The input voltage to the system will be the u(t) signal outputted by the pre-filter simulation.
- We have simulated with COMSOL, SPICE, and two homebrewed algorithms, but more work is necessary before presentation of final results.



Physical Circuit

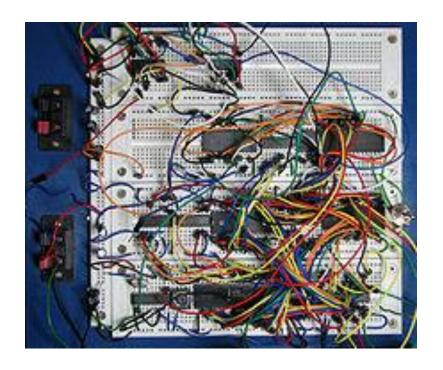- We would like to create a real circuit of what is modeled in SPICE and test it with the same inputs.
 - Need to find appropriately valued components





References

- M. Fliess, P. Martin, N. Petit, P. Rouchon, "Active signal restoration for the telegraph equation", in Proc. of the 38th IEEE Conf. on Decision and Control, 1999.
- ▶ J. Feldman, "Derivation of the Telegraph Equation", 2005.
- R. McCammon, "SPICE Simulation of Telegraph Lines by the Telegrapher's Method", 3M Communication Markets Div., 2010.

